



RV Educational Institutions[®]
RV College of Engineering[®]

Autonomous
Institution Affiliated
to Visvesvaraya
Technological
University, Belagavi

Approved by AICTE,
New Delhi



Go, change the world



18N23A1072

Academic year 2023-2024 (EVEN Sem)

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Date	14/05/24	Maximum Marks	50
Course Code	EE123AT	Duration	90 Min
Sem	2 nd sem	Test-1	
COURSE NAME: BASICS OF ELECTRICAL ENGINEERING			

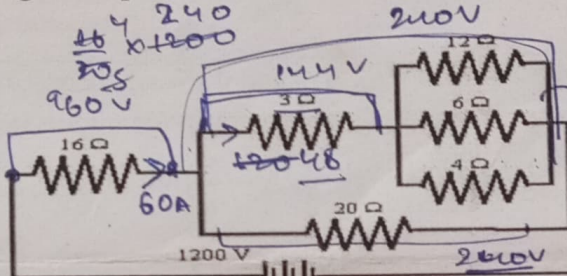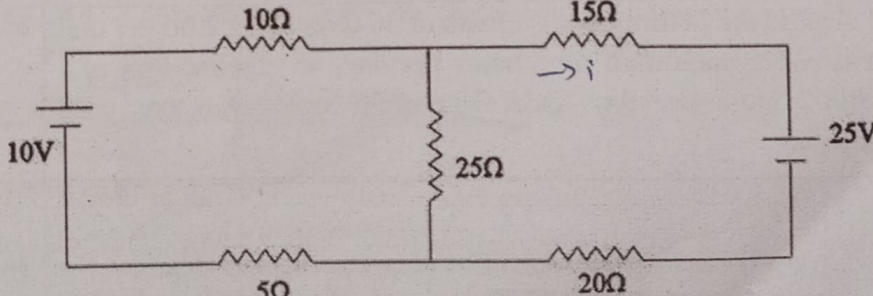Sl. No	Questions	Marks	CO	BT
1a)	<p>Find the equivalent resistance of the circuit shown. Find the voltage drop over, current through, and power dissipated by each resistor.</p>  <p>Handwritten calculations for 1a:</p> $\frac{16 \times 20}{16 + 20} = 11.43 \Omega$ $\frac{11.43 \times 20}{11.43 + 20} = 6.19 \Omega$ $\frac{6.19 \times 4}{6.19 + 4} = 4.2 \Omega$ $\frac{4.2 \times 6}{4.2 + 6} = 2.94 \Omega$ $\frac{2.94 \times 3}{2.94 + 3} = 1.64 \Omega$ $\frac{1.64 \times 20}{1.64 + 20} = 1.44 \Omega$ $R_{eq} = 16 + 1.44 = 17.44 \Omega$ $I = \frac{1200}{17.44} = 68.8 A$ $V_{16\Omega} = 1111.2 V$ $V_{3\Omega} = 206.4 V$ $V_{20\Omega} = 1376 V$ $V_{6\Omega} = 249.6 V$ $V_{4\Omega} = 166.4 V$ $P_{16\Omega} = 1111.2 W$ $P_{3\Omega} = 4272 W$ $P_{20\Omega} = 15936 W$ $P_{6\Omega} = 3792 W$ $P_{4\Omega} = 2528 W$	5	2	2
b)	<p>A 100W, 200V bulb is connected in series with a 60W bulb across a supply.</p> <p>Determine the following</p> <p>(i) Find the current drawn</p> <p>(ii) What will be the voltage across the 60W bulb</p> <p>(iii) Find the supply voltage</p>	5	2	1
2a)	<p>Calculate the branch current in 15 Ω resistor by applying Kirchhoff's law</p>  <p>Handwritten calculations for 2a:</p> $\frac{5 \times 60}{5 + 60} = 4.76 A$	5	2	2

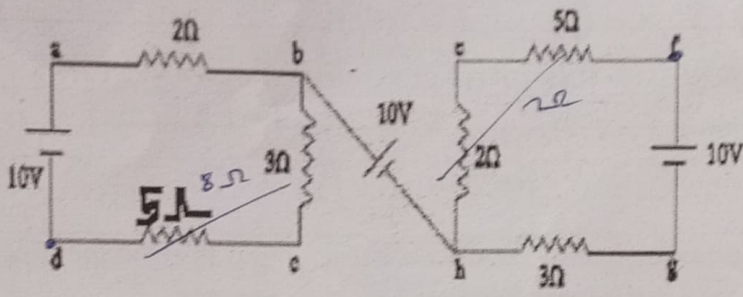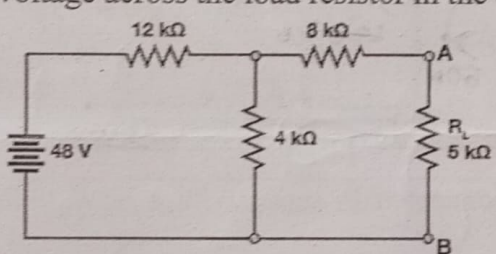6)	For the Circuit shown below determine voltages V_{df} .	5	2	2
				
3a)	Using Thevenin's Theorem find V_{TH} , R_{TH} and the load current I_L flowing through and load voltage across the load resistor in the circuit below.	5	3	3
				
b)	State and prove the Maximum Power Transfer theorem.	5	2	2
4a)	Mention any four precautions against Electric Shock.	4	3	1
b)	What is the necessity of earthing the electrical appliances? Explain with diagram plate earthing.	6	3	2
5a)	Illustrate how the power is transmitted and distributed through block diagrams.	4	2	2
b)	Calculate the electric bill at the end of a month of 30 days at Rs.2.00 per unit if 6 lamps of 40 watts each burn for 8 hours per day, an electric iron of 1 kW is used for 2 hours per day and 4 fans of 50 watts each are used for 10 hours per day.	6	4	3

BT-Blooms Taxonomy, CO-Course Outcomes, M-Marks

Marks Distribution	Particulars		CO1	CO2	CO3	CO4	BT1	BT2	BT3
	Test	Max Marks	00	29	15	06	09	30	11



Department of Electrical & Electronics Engineering

Basics of Electrical Engineering

Date	19 th June 2024	Maximum Marks	50	
Course Code	22ES24D	Duration	90 Mins	
Sem	II Semester	CIE -2		
Basics of Electrical Engineering				
Q.No	CIE - 2	Marks	COs	BT
1. a)	Derive expressions for Effective and Average value of an alternating quantity.	4	2	2
b)	An alternating current varying sinusoidally with a frequency of 50 Hz has an RMS value of 20 A. Write down the equation for the instantaneous value and find this value (a) 0.0025 second (b) 0.0125 second after passing through a positive maximum value. At what time, measured from a positive maximum value, will the instantaneous current be 14.14 A?	6	2	3
2. a)	Prove that in a series RL Circuit, Power consumed is $P = VI \cos \phi$ with all relevant equations, phasor diagram and Graphical representation.	5	2	3
b)	A current of 5 A flows through a non-inductive resistance in series with a choking coil when supplied at 250-V, 50-Hz. If the voltage across the resistance is 125 V and across the coil 200 V, calculate (a) impedance, reactance and resistance of the coil (b) the power absorbed by the coil and (c) the total power. Draw the vector diagram.	5	3	3
3. a)	A three-phase delta connected motor operating on a 400 V supply is delivering 25 HP at an efficiency of 0.87 and power factor of 0.42. Calculate the line current, phase current and the readings of two-watt meters connected to measure the input. Assume, 1hp=746 w.	6	3	3
b)	Explain the advantages of 3 phase circuits over single phase circuits.	4	1	2
4. a)	Arrive at the Voltage and Current expressions for 2 types of connections of a 3-phase circuit.	5	1	2
b)	A balanced, three phase, star connected load is fed from a 400V, three phase, 50Hz supply. The current per phase is 25 A(lagging) and the total active power absorbed by the load is 13.856 kW.	5	3	3

Star

$$E_L = \sqrt{3} E_{ph}$$

del

$$I_{ph} = \sqrt{3} I_L$$

**Department of Electrical & Electronics Engineering**

	Determine the resistance and inductance of the load per phase, the total reactive power and total apparent power.			
5. a) <i>calc</i>	Prove that, the readings of the wattmeter's are in terms of $\cos(30+\phi)$ and $\cos(30-\phi)$ while measuring the power of a three-phase circuit. Mention the status of two wattmeter's at power factors: 1, 0.5 and 0 respectively.	6	2	3
b) /	Input power to a three-phase circuit was measured by two wattmeter method. The readings were 3kW and 1.5kW. Determine the total power consumed and the power factor of the balanced three phase circuit.	4	3	2

BT-Blooms Taxonomy, CO-Course Outcomes, M-Marks

Marks Distribution	Particulars		CO1	CO2	CO3	CO4	L1	L2	L3	L4	L5	L6
	Test	Max Marks	9	21	20	-	-	17	33	-	-	-



RV College of Engineering®

Mysore Road, RV Vidyaniketan Post,
Bengaluru - 560059, Karnataka, India

NBA Accredited (UG & PG)

hod. ee@rvce.edu.in
www.rvce.edu.in
Tel: 080-68188192

Department of Electrical & Electronics Engineering

Basics of Electrical Engineering

Date	2 nd July 2024	Maximum Marks	60
Course Code	EE123ATD	Duration	110 Mins
Sem	II Semester	Improvement Test	
Basics of Electrical Engineering			

PART - A				
Q.No	Questions	Marks	COs	BT
1.	Define voltage regulation of a transformer.	2	CO2	L1
2.	A 11000 / 220V , 50Hz, 1-phase transformer takes a current of 20A, if the number of turns on the primary side is 1000. The primary and secondary currents are $I_1 = \text{-----}$ and $I_2 = \text{-----}$.	2	CO2	L2
3.	Mention the constant and variable losses in transformers, and also write the equation for the same.	2	CO1	L1
4.	The current in a circuit is $(8 - j10)A$, when the applied voltage is $(50 + j25)V$. determine the impedance and power factor of the circuit.	2	CO1	L2
5.	The equation for an alternating current is given by $i = 28.28 \sin(314t + 30^\circ) A$. Find its r.m.s, frequency and phase angle	2	CO2	L1



RV College of Engineering®

Mysore Road, RV Vidyaniketan Post,
Bengaluru - 560059, Karnataka, India

NBA Accredited (UG & PG)

hod.ee@rvce.edu.in
www.rvce.edu.in
Tel: 080-68188192

Department of Electrical & Electronics Engineering

PART - B




Q.No	Questions	Marks	COs	BT
1. a)	Derive the E.M.F equation of a transformer.	04	02	02
b)	A 600 kVA transformer has an efficiency of 92% at full-load, unity power factor and at half-load, 0.9 power factor. Determine its efficiency at 75% of full-load and 0.9 power factor	06	03	03
2. a)	Explain the constructional details of core and shell type transformer.	05	02	01
b)	A single phase, 20 kVA transformer has 1000 primary turns and 2500 secondary turns. The net cross-sectional area of the core is 100 cm^2 . When the primary winding is connected to 500V, 50 Hz supply. Calculate i) The maximum value of the flux density in the core ii) The voltage induced in the secondary winding iii) The primary and secondary full load currents	05	02	02
3. a)	A coil of power factor 0.6 is in series with $100 \mu\text{F}$. When connected to a 50Hz supply, the potential difference (p.d) across the coil is equal to the p.d across the capacitor. Find the resistance and inductance of the coil.	05	02	02
b)	Show that a pure inductance does not consume any power. Draw the waveforms of voltage, current and power, when a sinusoidal voltage is applied to a pure inductance.	05	02	02
4. a)	Define the following terms: i) Instantaneous value ii) Amplitude iii) Form factor and iv) Peak factor	04	01	01
b)	A current $i = 10 \sin(314t - 10^\circ)$ A produces a potential drop $v = 220 \sin(314t + 20^\circ)$ V in a circuit. Find the values of the passive elements, assuming a series combination of only two passive elements is supplied from a source.	06	02	02
5. a)	Derive an equation for the power consumed by an R-C series circuit. Draw the waveforms of voltage, current, and power.	05	02	01
b)	An inductive coil takes a current of 33.24 A from 230V, 50Hz supply. If the resistance of the coil is 6Ω . Calculate the inductance of the coil and the power taken by the coil.	05	02	02





Marks Distribution	Particulars		CO1	CO2	CO3	CO4	L1	L2	L3	L4	L5	L6
	Test	Max Marks	08	46	06	-	20	34	06	-	-	-





Academic year 2023-2024 (EVEN Sem)


DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING


Date	13/05/24	Maximum Marks	50
Course Code	EE123AT	Duration	90 Min
Sem	2 nd sem	Test-1	
COURSE NAME: BASICS OF ELECTRICAL ENGINEERING			

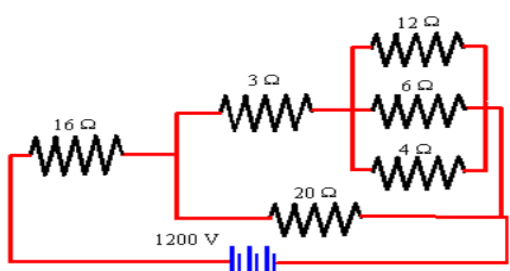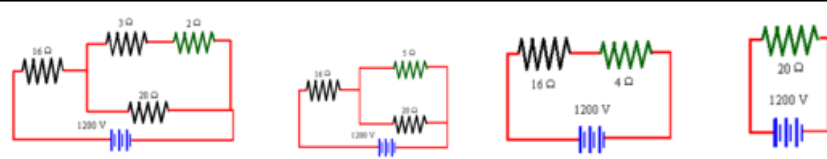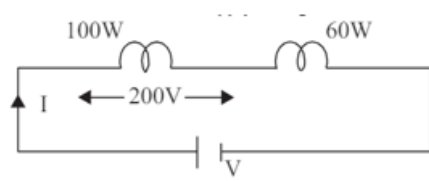Sl. No	Questions	Marks	CO																																
1a)	Find the equivalent resistance of the circuit shown . Find the voltage drop over, current through, and power dissipated by each resistor. 	5	2																																
sol	 <table border="1"> <thead> <tr> <th>Resistor (Ω)</th><th>V (Volts)</th><th>I (Amps)</th><th>P (Watts)</th></tr> </thead> <tbody> <tr><td>16</td><td>960</td><td>60</td><td>57600</td></tr> <tr><td>20</td><td>240</td><td>12</td><td>2880</td></tr> <tr><td>3</td><td>144</td><td>48</td><td>6912</td></tr> <tr><td>12</td><td>96</td><td>8</td><td>768</td></tr> <tr><td>6</td><td>96</td><td>16</td><td>1536</td></tr> <tr><td>4</td><td>96</td><td>24</td><td>2304</td></tr> <tr><td>20</td><td>1200</td><td>60</td><td>72000</td></tr> </tbody> </table>	Resistor (Ω)	V (Volts)	I (Amps)	P (Watts)	16	960	60	57600	20	240	12	2880	3	144	48	6912	12	96	8	768	6	96	16	1536	4	96	24	2304	20	1200	60	72000		
Resistor (Ω)	V (Volts)	I (Amps)	P (Watts)																																
16	960	60	57600																																
20	240	12	2880																																
3	144	48	6912																																
12	96	8	768																																
6	96	16	1536																																
4	96	24	2304																																
20	1200	60	72000																																
b)	A 100W, 200V bulb is put in series with a 60W bulb across a supply. What will be the current drawn? What will be the voltage across the 60W bulb? What will be the supply voltage?	5	2																																
	<p>Power dissipated in the first bulb, $P_1 = V_1 I$ Current, $I = P_1 / V_1 = 100/200 = 0.5 \text{ A}$ Power dissipated in the second bulb, $P_2 = V_2 I$ Voltage across the 60 W bulb,</p> $V = \frac{P_2}{I} = \frac{60}{0.5} = 120V$ <p>The supply voltage, $V = V_1 + V_2 = 200 + 120$ $V = 320V$</p> <p>The supply voltage, $V = 320 \text{ V}.$</p> 																																		
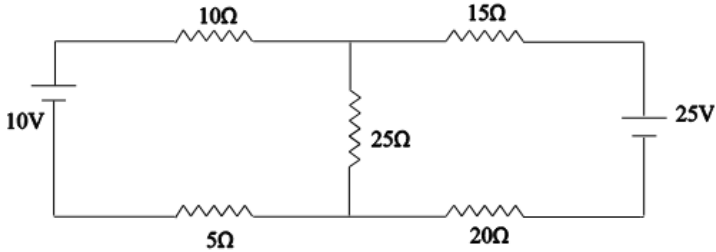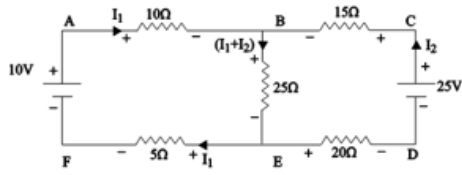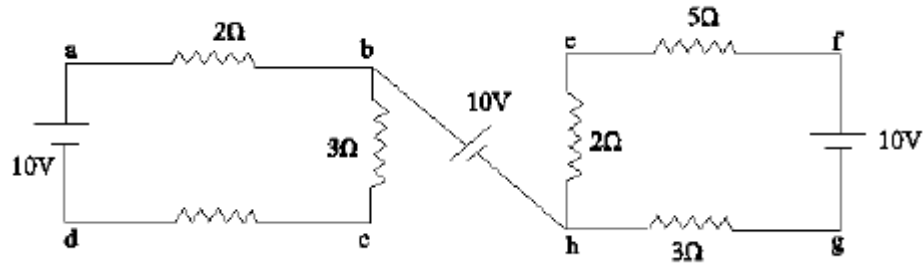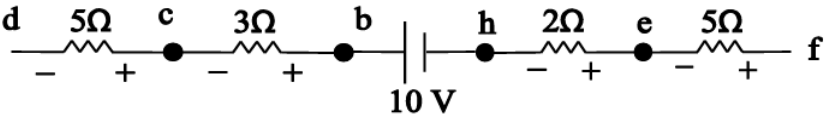
<p>2a)</p>	<p>Calculate the branch current in $15\ \Omega$ resistor by applying Kirchhoff's law</p> 	<p>5</p>	<p>2</p>
	<div style="display: flex; justify-content: space-between;"> <div style="width: 45%;">  <p>Consider the loop ABEFA & apply KVL in CLK wise</p> $10 - 10I_1 - 25(I_1 + I_2) - 5I_1 = 0$ $10 - 10I_1 - 25I_1 - 25I_2 - 5I_1 = 0$ $-40I_1 - 25I_2 + 10 = 0$ $40I_1 + 25I_2 = 10$ <p>(1)</p> </div> <div style="width: 45%;"> <p>Consider the loop BCDEB and Apply KVL in CLK wise direction</p> $15I_2 - 25 + 20I_2 + 25(I_1 + I_2) = 0$ $15I_2 - 25 + 20I_2 + 25(I_1 + I_2) = 0$ $15I_2 - 25 + 20I_2 + 25I_1 + 25I_2 = 0$ $25I_1 + 60I_2 - 25 = 0$ $25I_1 + 60I_2 = 25 \dots\dots\dots(2)$ <p>$I_2 = 0.42$ Amps.</p> <p>Current in $15\ \Omega$ resistor is 0.42Amps.</p> </div> </div>	<p>5</p>	<p>2</p>
<p>b)</p>	<p>For the Circuit shown below determine voltages V_{df}.</p>  <p>Apply KVL to loop abcd</p> $10 - 2I_1 - 3I_1 - 5I_1 = 0$ $-10I_1 = -10$ $I_1 = 1 \text{ Amps}$ <p>Apply KVL to loop efgh</p> $5I_2 - 10 + 3I_2 + 2I_2 = 0$ $10I_2 = 10$ $I_2 = 1 \text{ Amps}$  $V_{df} = -5(I_1 - 3I_1 + 10 + 2I_2 + 5I_2)$ $V_{df} = -5 - 3 + 10 + 2 + 5$ $V_{df} = 9 \text{ Volts.}$ <p>$V_{df} = -9 \text{ Volts}$ [because - sign on d side + on f side]</p>	<p>5</p>	<p>2</p>

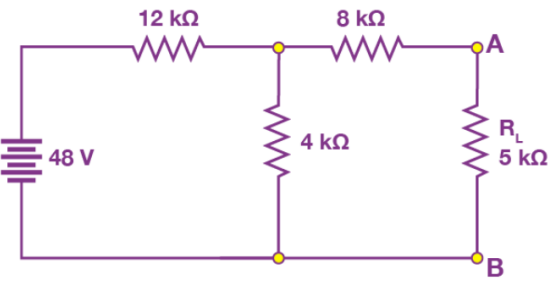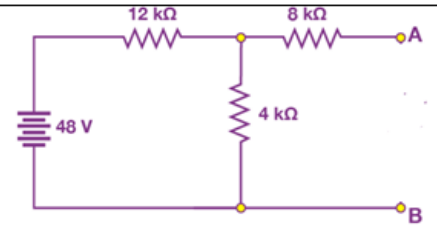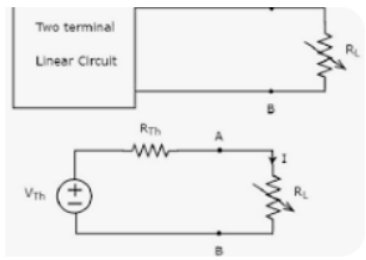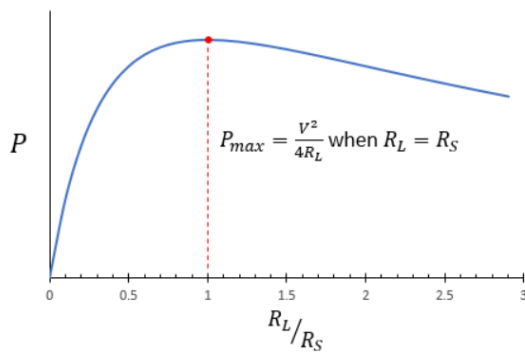3a)	<p>Using Thevenin's Theorem find V_{TH}, R_{TH} and the load current I_L flowing through and load voltage across the load resistor in the circuit below.</p> 	5	3
	 <p>Remove the 5 kΩ from the circuit. Measure the open-circuit voltage. This will give you the Thevenin's voltage (V_{TH}).</p> <p>$I = 48 \text{ V} / (12 \text{ k}\Omega + 4 \text{ k}\Omega) = 3 \text{ mA}$</p> <p>Thevenin's Resistance R_{TH} calculated as follows:</p> $8 \text{ k}\Omega + (4 \text{ k}\Omega \parallel 12 \text{ k}\Omega)$ $R_{TH} = 8 \text{ k}\Omega + [(4 \text{ k}\Omega \times 12 \text{ k}\Omega) / (4 \text{ k}\Omega + 12 \text{ k}\Omega)]$ $R_{TH} = 8 \text{ k}\Omega + 3 \text{ k}\Omega$ $R_{TH} = 11 \text{ k}\Omega$		
b)	<p>State and prove Maximum power transfer theorem.</p>   <p>The maximum power transfer theorem states that the power delivered to the load resistor is maximized when the load resistance is equal to the series resistance. This can be calculated by taking the derivative of the power equation with respect to the load resistance and calculating the critical point.</p>	5	2
4a)	<p>Mention any eight precautions against Electric Shock.</p> <ol style="list-style-type: none"> 1. The first step of electrical safety, avoid water at all times when working with electricity. Never touch or try repairing any electrical equipment or circuits with wet hands. It increases the conductivity of the electric current. 2. Never use equipment with frayed cords, damaged insulation, or broken plugs. 3. If you are working on any receptacle at your home then always turn off the mains. It is also a good idea to put up a sign on the service panel so that nobody turns the main switch ON by accident. 4. Always use insulated tools while working. 	4	3


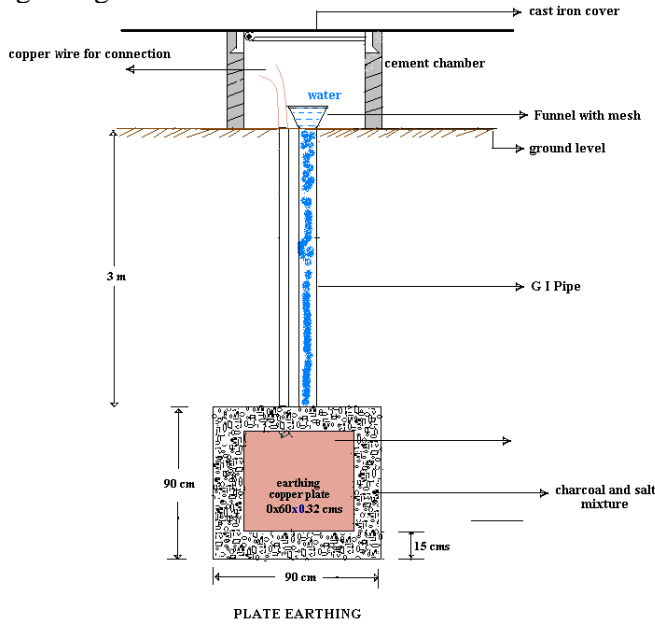
	<p>5. Electrical hazards include exposed energized parts and unguarded electrical equipment which may become energized unexpectedly. Such equipment always carries warning signs like “Shock Risk”.</p> <p>6. Always use appropriate insulated rubber gloves and goggles while working on any branch circuit or any other electrical circuit.</p> <p>7. Never try repairing energized equipment. Always check that it is de-energized first by using a tester.</p> <p>8. Never use an aluminum or steel ladder if you are working on any receptacle at height in your home. An electrical surge will ground you and the whole electric current will pass through your body. Use a bamboo, wooden or a fiberglass ladder instead.</p>		
b)	<p>What is the necessity of earthing the electrical appliances? Explain with diagram plate earthing.</p> <p>Necessity of Earthing:</p> <ol style="list-style-type: none"> 1. To protect the operating personnel from danger of shock in case they come in contact with the charged frame due to defective insulation. 2. To maintain the line voltage constant under unbalanced load condition. 3. Protection of the equipments 4. Protection of large buildings and all machines fed from overhead lines against lightning. 	6	3
5a)	Explain the concept of power transmission and distribution through block diagrams.	4	2



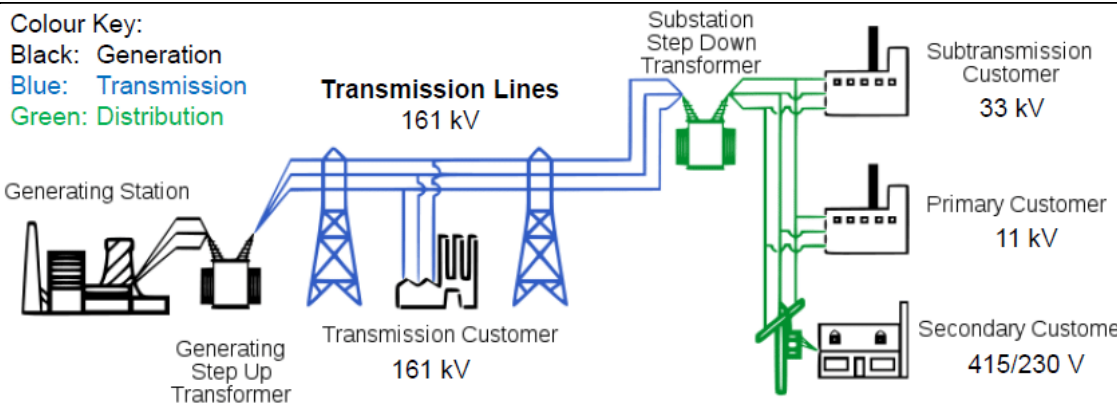
	<p>Colour Key: Black: Generation Blue: Transmission Green: Distribution</p> 																											
b)	Calculate the electric bill at the end of a month of 30 days at Rs.2.00 per unit if 6 lamps of 40 watt each burn for 8 hours per day, an electric iron of 1 kW is used for 2 hours per day and 4 fans of 50 watt each are used for 10 hours per day.	6	4																									
	<table><tr><th>Name of the Appliance</th><th>Power Rating (W)</th><th>Avg. Daily Usage Hrs</th><th>No. of Appliances</th><th>Daily Energy Required (Wh)</th></tr><tr><td>lamps</td><td>40</td><td>8</td><td>6</td><td>1920</td></tr><tr><td>electric</td><td>1kw</td><td>2</td><td>1</td><td>2000</td></tr><tr><td>fan</td><td>50</td><td>10</td><td>4</td><td>2000</td></tr><tr><td colspan="4">Total Energy</td><td>5920Wh</td></tr></table> <p>Total energy consumed per day $E_{total}=E_1+E_2+E_3$ $=1920+2000+2000=5920 \text{ Wh}$ 5.920 kWh or units Total energy consumed per month $=30\times E_{total}$ $=30\times 5.92 = 177.60 \text{ kWh or 177.60 units}$ Bill for one month $=\text{Rate/unit}\times\text{units}=(\text{Rs.2.00/unit})\times(177.60 \text{ units})$ $=\text{Rs.355.20}$ So the electric bill at the end of a month will be Rs.355.20</p>	Name of the Appliance	Power Rating (W)	Avg. Daily Usage Hrs	No. of Appliances	Daily Energy Required (Wh)	lamps	40	8	6	1920	electric	1kw	2	1	2000	fan	50	10	4	2000	Total Energy				5920Wh		
Name of the Appliance	Power Rating (W)	Avg. Daily Usage Hrs	No. of Appliances	Daily Energy Required (Wh)																								
lamps	40	8	6	1920																								
electric	1kw	2	1	2000																								
fan	50	10	4	2000																								
Total Energy				5920Wh																								

SCHEME AND SOLUTION

CIE-2

BASICS OF ELECTRICAL ENGINEERING(EE123ATD)

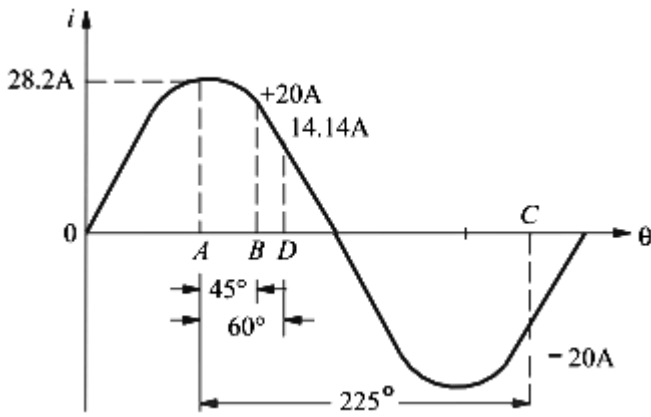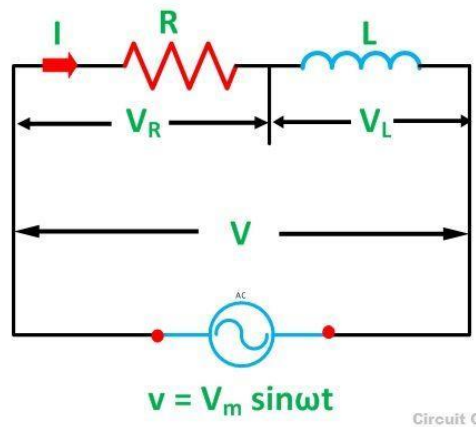Q.NO	SOLUTION	Marks
1.a	$I_{RMS} = 0.707 I_M$, $I_{AV} = 0.637 I_M$ -----04M	04
b	 <p style="text-align: right;">-----06M</p> <p> $I_m = 20\sqrt{2} = 28.2 \text{ A}$, $\omega = 2\pi \times 50 = 100 \pi \text{ rad/s}$. $i = 28.2 \sin 100 \pi t$ ampere </p> <p>(i) When $t = 0.0025$ second $i = 28.2 \cos 100\pi \times 0.0025$...angle in radian = $28.2 \cos 100 \times 180 \times 0.0025$...angle in degrees = $28.2 \cos 45^\circ = 20 \text{ A}$...point</p> <p>(ii) (ii) When $t = 0.0125$ second $i = 28.2 \cos 100 \times 180 \times 0.0125 = 28.2 \cos 225^\circ = 28.2 \times (1/\sqrt{2}) = -20 \text{ A}$...point</p> <p>(iii) (iii) Here $i = 14.14 \text{ A} \therefore 14.14 = 28.2 \cos 100 \times 180 t \therefore \cos 100 \times 180 t = 1/2$ or $100 \times 180 t = \cos^{-1}(0.5) = 60^\circ$, $t = 1/300$ second ...point D</p>	06
2.a	 <p style="text-align: center;">$v = V_m \sin \omega t$</p> <p style="text-align: right;">Circuit Globe</p> <p> $V_R = IR$ and $V_L = I X_L$ where $X_L = 2\pi f L$ </p> $V = \sqrt{(V_R)^2 + (V_L)^2} = \sqrt{(IR)^2 + (IX_L)^2}$ $V = I \sqrt{R^2 + X_L^2} \quad \text{or}$ $I = \frac{V}{Z}$	05

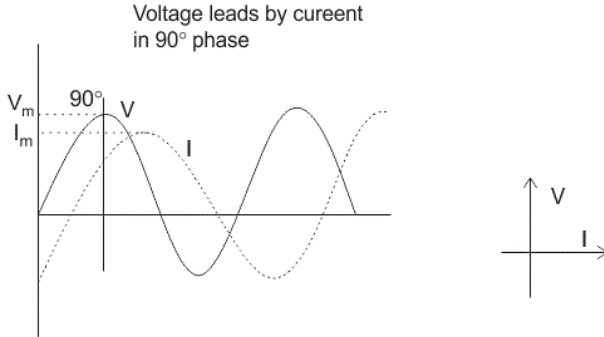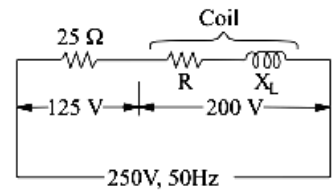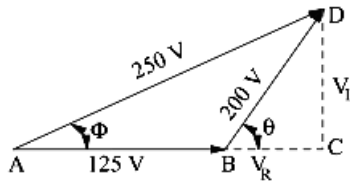	<p>Where, $z = \sqrt{R^2 + X_L^2}$</p> <p>$P = \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos\phi - \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(2\omega t - \phi) \text{ or}$</p> <p>$P = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos\phi - \text{Zero or}$</p> <p>$P = V_{r.m.s} I_{r.m.s} \cos\phi = VI \cos\phi$</p> <p>Voltage leads by current in 90° phase</p> 	
b.	  <p>$BC^2 + CD^2 = 200^2 \dots(i)$ $(125 + BC)^2 + CD^2 = 250^2 \dots(ii)$ Subtracting Eq. (i) from (ii), we get, $(125 + BC)^2 - BC^2 = 250^2 - 200^2$</p> <p>$\therefore BC = 27.5V$; $CD = \sqrt{(200^2 - 27.5^2)} = 198.1V$</p> <p>(i) Coil impedance $= 200/5 = 40 \Omega$</p> <p>$V_R = IR = BC$ or $5R = 27.5$</p> <p>$\therefore P = 27.5/5 = 5.5 \Omega$ Also $V_L = I \cdot X_L = CD = 198.1$</p> <p>$\therefore X_L = 198.1/5 = 39.62 \Omega$ or $X_L = (40^2 - 5.5^2) = 39.62\Omega$</p> <p>(ii) Power absorbed by the coil is $= I^2 R = 5^2 \times 5.5 = 137.5 W$</p> <p>Also $P = 200 \times 5 \times 27.5/200 = 137.5 W$</p> <p>(iii) Total power $= VI \cos \phi = 250 \times 5 \times AC/AD = 250 \times 5 \times 152.5/250 = 762.5 W$</p>	05
3.a	$I_L = 73.64A$, $I_{PH} = 42.53A$, $W_1 = - 2.65 KW$, $W_2 = 24.08 KW$	06
b	Any 4 advantages	04
4.a	Star : $E_L = \sqrt{3} E_{ph}$, $I_L = I_{ph}$, Delta: $I_L = \sqrt{3} I_{ph}$, $E_L = E_{ph}$	05
b	$Z_{ph} = 9.23 \text{ ohm}$, $R = 7.384 \text{ ohm}$, $X_L = 5.538 \text{ ohm}$, $L = 0.0176H$ $Q = 10392.30$, $S = 17320.5$	05
5.a	i) Unity pf $= W_1 = W_2$ ii) 0.5 pf $= W_1 = 0$, $W_2 = 0.866$ iii) zero pf $= W_1 = -0.5$, $W_2 = +0.5$	06
b	$P = 4.5 KW$, $Pf = 0.866$	04

**CHEME AND SOLUATION
IMPROVEMENT TEST
BASICS OF ELECTRICAL ENGINEERING(EE123ATD)**

SI.No	Quiz-2
1	“ The rise in secondary terminal voltage from no-load to full-load keeping the primary voltage constant”
2	$I_1 = 20\text{A}$, $I_2 = 1000\text{A}$
3	Core or Iron loss : $W_h = P B_{\max}^{1.6} f$ watt , $W_e = Q B_{\max}^2 f^2$ watt Copper or I^2R loss : $I_1^2 R_1 + I_2^2 R_2$
4	$I = 12.80 \angle -51.34^\circ\text{A}$, $V = 55.90 \angle 26.60^\circ\text{V}$ $Z = 4.30 \text{ Ohm}$, $\text{Pf} = 0.21$
5	$I_{\text{RMS}} = 20 \text{ A}$, $f = 50\text{Hz}$, $\Phi = 30^\circ$

SCHEME AND SOLUTION

IMPROVEMENT TEST

BASICS OF ELECTRICAL ENGINEERING(EE123ATD)

Q.NO	SOLUTION	Marks
1.a	$E_1 = 4.44 f \Phi_m N_1$, $E_2 = 4.44 f \Phi_m N_2$ -----02* 02M	04
b	$W_I = 13.91KW$, $W_{CU} = 38.26KW$ -----04M $\eta = 91.96\%$ -----02M	06
2.a	Diagram ----02M, Explanation ----03M	05
b.	$B_m = 0.225 \text{ Wb / m}^2$ ----01M $E_2 = 1250V$ ----02M $I_1 = 40A$, $I_2 = 16A$ -----02M	05
3.a	$Z = 31.83 \text{ ohm}$ ----02M, $R = 19.09 \text{ ohm}$ -----01M, $X_L = 25.46 \text{ ohm}$ ---01M, $L = 0.081H$ —01M	05
b	Diagram ---01M , Derivation ----03M $P = 0$, Waveform----01M	05
4.a	Each definition -----01*04---04M	04
b	$Z = 22 \angle 30^\circ \text{ ohm}$ -----02M, $R = 19.05 \text{ ohm}$ ----02M, $X_L = 11 \text{ ohm}$ ---01M $L = 0.035H$ -----01M	06
5.a	Diagram—01M, Derivation ---03M $P = V \cos \Phi$, Waveform---01M	05
b	$Z = 6.92 \text{ ohm}$ ---01M $X_L = 3.45 \text{ ohm}$ ----01M , $L = 10.98 \text{ mH}$ ----01M, $P = 6629 \text{ wattts}$ ---02M	05