

**RV COLLEGE OF ENGINEERING\***  
(An Autonomous Institution affiliated to VTU)  
I Semester B. E. Examinations May-2023

Common to AI/AS/BT/CH/CS/CY/CD/EE/IM/IS/ME/CV

**PRINCIPLES OF ELECTRONICS ENGINEERING (ELECTIVE)**

Time: 03 Hours

Maximum Marks: 100

Instructions to candidates:

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. Question number 2 is compulsory. Choose any one full question from 3 or 4, 5 or 6, 7 or 8 and 9 or 10.

**PART-A**

1	1.1	The output voltage of a regulated DC power supply changes from 20V to 19.7V when the load is increased from zero to maximum. Then the load regulation is _____.	02
	1.2	A transistor amplifier connected in CE mode has the value of $\beta$ as 100 and $I_B$ as $50\mu A$ , then the value of $I_E$ and $\alpha$ are _____ and _____ respectively.	02
	1.3	An amplifier has a voltage gain of 100 at 1KHz. The gain falls by 6dB at 1MHz. If the input is 3mW at 2MHz, then the output voltage is _____.	02
	1.4	In an RC phase shift oscillator using an ideal voltage amplifier, the frequency of oscillation is 2KHz. If $R = 6.25\Omega$ , the value of C is _____.	01
	1.5	A non-inverting amplifier using an op-amp has $R_i = 10K\Omega$ and $R_f = 40K\Omega$ . The closed loop gain is _____.	01
	1.6	An operational amplifier has a differential gain of 100 and a common mode gain of 0.01. Then its CMRR is _____ dB.	01
	1.7	The ones's complement of 01011 is _____.	01
	1.8	The decimal equivalent of $(321)_8$ is _____.	01
	1.9	The minimum number of NOR gates required to realize XOR gates is _____.	01
	1.10	For an AM signal, the bandwidth is 10KHz and the highest frequency component present is 705KHz. The carrier frequency used for this AM signal is _____.	02
	1.11	A carrier of peak voltage 15V is used to transmit a message signal. If the modulation index is 70%, then the peak voltage of the modulating signal is _____.	01
	1.12	The carrier amplitude after AM varies between 4V and 1V. The depth of modulation is _____.	01
	1.13	A 400W carrier is modulated to a depth of 75%. Assuming the modulating signal to be sinusoidal, the total power in the amplitude-modulated wave is _____.	01
	1.14	A part of the transducer which responds to a change in the physical phenomenon is called _____.	01

1.15	The elements which exhibit Piezo-electric qualities are called	01
1.16	A Hall effect transducer is used to measure a magnetic field of $0.5 \text{ wb/m}^2$ , Bismuth slab of $2 \text{ mm}$ thickness with a Hall coefficient of $-1 \times 10^{-6} \text{ Vm/(A - wb/m}^2)$ , and current $3 \text{ A}$ is used. Then the corresponding output voltage is	01

**PART-B**

2	<p>a Draw the circuit of a full wave bridge rectifier and describe its working with suitable Waveforms.</p> <p>b In a Zener regulator circuit shown in Fig 2b, design the value of <math>R</math>, so that the circuit performs satisfactorily under all given conditions.  <math>I_{zmin} = 5 \text{ mA}</math>, <math>P_{d(max)} = 2.5 \text{ W}</math> and <math>V_z = 5.6 \text{ V}</math>.</p> <div data-bbox="460 619 1031 850" data-label="Diagram"> </div> <p align="center">Fig 2b</p> <p>c An amplifier having a power gain of <math>17 \text{ dB}</math> delivers a power output of <math>40 \text{ W}</math> to a load of <math>1 \text{ k}\Omega</math>. Calculate  i) The input power needed  ii) The input voltage needed  Assume voltage gain of the amplifier is <math>38 \text{ dB}</math>.</p>	<p>06</p> <p>06</p> <p>04</p>
3	<p>a Draw the circuit of an integrator using an op-amp and derive the expression for the output voltage.</p> <p>b Calculate the output voltage of a three-input summing amplifier shown in Fig 3b</p> <div data-bbox="452 1281 1038 1522" data-label="Diagram"> </div> <p align="center">Fig 3b</p> <p>c Mention any four advantages of negative feedback.</p> <p align="center"><b>OR</b></p>	<p>06</p> <p>04</p>
4	<p>a Explain the operation of <math>RC</math> phase shift oscillator with a neat diagram and also mention the gain equation.</p> <p>b Design a scaling adder circuit using an op-amp to obtain an output expression. <math>V_o = -(3V_1 + 4V_2 + 5V_3)</math> where <math>V_1, V_2, V_3</math> are the inputs. Assume the value of feedback resistor as <math>10 \text{ k}\Omega</math>.</p> <p>c Draw the circuit of a differentiator using an op-amp. Derive the expression for the output voltage.</p>	<p>06</p> <p>05</p> <p>05</p>



5	a	Write the truth table for <i>SUM</i> and <i>CARRYOUT</i> of a full adder. From the truth table, obtain the logic expressions for the same and then realize the full adder using 2 half adders.	05
	b	Simplify the logic expression and implement the logic circuit using <i>NOR</i> Gate.	05
	c	$Y = (A + \bar{B} + C)(\bar{A} + B + C)(A + B)$ Simplify the logic expression using <i>K</i> map and implement the logic circuit using <i>NAND</i> Gate. $F(A, B, C, D) = \Sigma m(0, 1, 3, 5, 7, 8, 9, 11, 13, 15)$	06
<b>OR</b>			
6	a	Simplify the logic expression and implement the logic circuit using <i>NAND</i> Gate	06
	b	$Y = (A + \bar{B} + C)(\bar{A} + B + \bar{C})(A + \bar{B})$ Simplify the logic expression using <i>K</i> map and implement the logic circuit using basic Gates.	06
	c	$F(A, B, C, D) = \Sigma m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$ Realize the <i>EX – NOR</i> function using a minimum number of <i>NOR</i> gates only.	04
7	a	With the help of a neat block diagram explain the working of a Superheterodyne receiver.	06
	b	A carrier of 2MHz has 1KW of its power amplitude modulated with a sinusoidal signal of 2KHz. The depth of modulation is 60%. Calculate the sideband frequencies, bandwidth, power in sidebands, total power, and efficiency.	06
	c	Write any four differences between Harvard and Von-Neumann <i>CPU</i> architecture.	04
<b>OR</b>			
8	a	With the help of a block diagram, explain the working of a digital communication system.	06
	b	For an <i>AM</i> signal $V_{AM} = 10(1 + 0.5\sin 6280t)\sin(62.8 \times 10^6t)$ . Calculate the sideband frequencies, bandwidth, amplitude of each sideband, Total power, and efficiency.	06
	c	List any four differences between <i>RISC</i> and <i>CISC</i> .	04
9	a	With the help of a neat diagram, discuss the working principle of <i>LVDT</i> .	08
	b	Explain the working principle of ultrasonic sensors and Humidity sensors mentioning their respective applications.	08
<b>OR</b>			
10	a	Explain the working of a piezo-Electric Transducer with relevant equations.	06
	b	Briefly explain the working of capacitive transducers.	06
	c	Mention any four differences between active and passive transducers.	04